

Section 1 - Simplifying Expressions

Wednesday, June 19, 2019 11:18 AM

• SECTION 1:

• SIMPLIFYING EQUATIONS •

- ALWAYS SIMPLIFY BEFORE MAKING A CIRCUIT

- USE PROPERTIES TO SIMPLIFY

$$r = ab'c' + ab'c'$$

$$r = ac'(b + b')$$

$$r = ac'(1)$$

$$r = ac'$$

KMAPS

- KARNAUGH MAP
- A MAP OF A FUNCTION

		b	
		0	1
a	0	$a'b'$	$a'b$
	1	ab'	ab

$$y = a'b' + ab'$$

		b	
		0	1
a	0	$a'b'$	0
	1	ab'	0



		b	
		0	1
a	0	1	0
	1	1	0

- EACH BOX IS A MINTERM
- You can simplify an eq using circles in a kmap

	b	
a	0	1
0	1	0
1	1	0

$$x = a'b' + ab'$$

$$x = (a' + a)b'$$

$$x = (1)b'$$

$$x = b'$$

RULES REGARDING CIRCLES

- COVER EVERY 1 AT LEAST ONCE
↳ ADD TERM TO EXPRESSION
- USE FEWEST + LARGEST CIRCLES POSSIBLE

MORE VARIABLES: MORE FUN

3 VARIABLES

		bc			
		00	01	11	10
a	0	$a'b'c'$	$a'b'c$	$a'bc$	$a'bc'$
	1	$ab'c'$	$ab'c$	abc	abc'

$a'b$

b'

4 VARIABLES

		cd			
		00	01	11	10
ab	00	0	1	0	0
	01	0	1	0	0
	11	1	1	1	1
	10	0	0	1	1

$a'c'd$

ab

bc

- THE LARGER THE CIRCLE - THE FEWER TERMS

DE MORGAN'S LAWS

$$\text{OR} \mid (a \vee b)' = a' \wedge b'$$

$$\text{AND} \mid (a \wedge b)' = a' \vee b'$$

WHEN AN OPERATION IS 'NOT', FLIP
THE SIGN & NOT EACH ITEM

XOR / XNOR

$$y = a \oplus b$$


a	b	y
0	0	0
0	1	1
1	0	1
1	1	0



$$a \oplus b = a'b + ab'$$

MORE GATES? NO PROBLEM

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

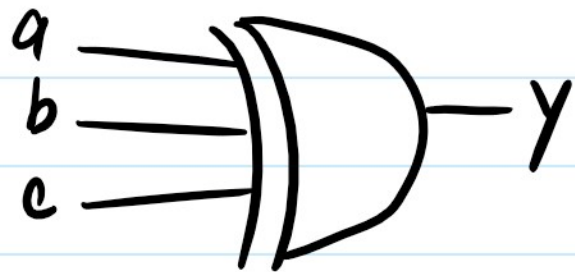


• ODD # OF 1s

NAND


NAND is NOT AND :O

"GASPS IN SPANISH!"


a	b	y
0	0	1
0	1	1
1	0	1
1	1	0

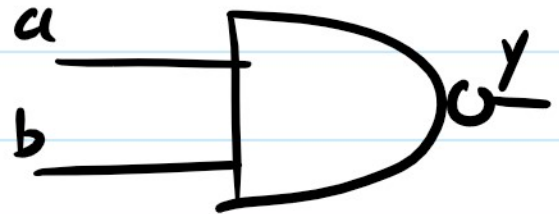

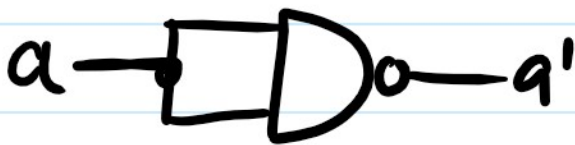
• IS A UNIVERSAL GATE: CAN MAKE ANY GATE FROM THESE



NOT
 $(aa)' = a' + a' = a'$

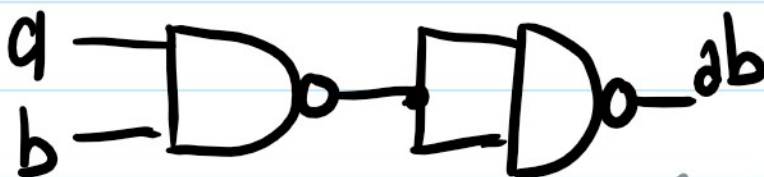

AND
 $((ab)')' = (ab)'' = ab$

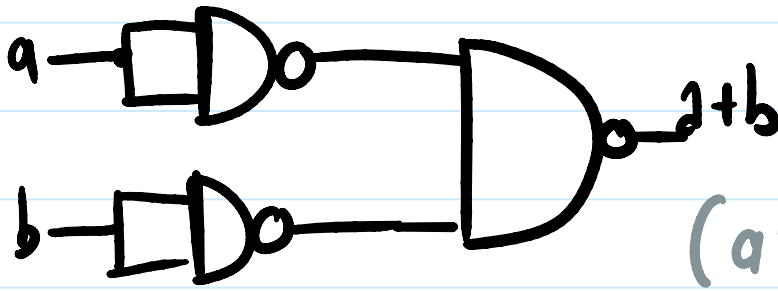

OR

$$(a'b')' = a'' + b'' = a + b$$

NOR

- NOR IS NOT OR :O
"CLASPS IN SPANISH"

- UNIVERSAL GATE

a	b	y
0	0	1
0	1	0
1	0	0
1	1	0




NOT

$$(a + a)' = a'a' = a'$$



OR

$$((a+b)')' = (a+b) = a+b$$

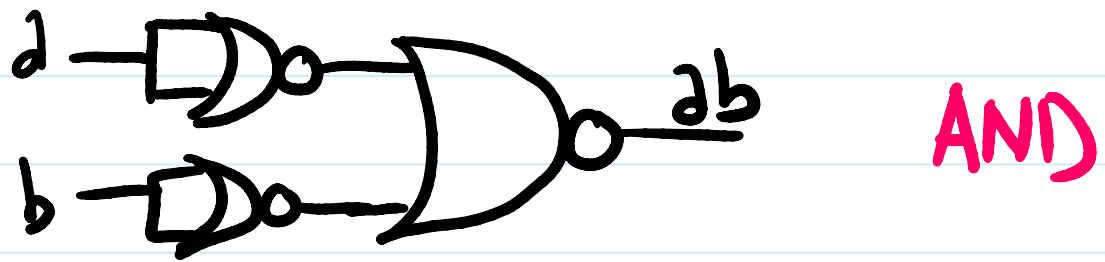

$$(a' + b')' = a''b'' = ab$$