

BOOLEAN LOGIC

"A TALE OF TWO GEORGES"

GEORGE BOOLE

- WROTE *Laws of Thought*
 - about how we think
 - Based around statements + if they're true or false
 - We can operate on these T/F variables

GEORGE STIBITZ

- "I bet I can use a bunch of fuckin relays to add numbers"
- STIBITZ MODEL K
 - He built it in his Kitchen: hence model K
 - A/B are switches so T/F + 0/1 and the two lights turn off and on to be 0/1

HOW TO AVOID BEING POISONED

```
if (wife loves Me && wife Makes Food)
{
```

```
    me.eat(wife Food);
```

```
    health = me.checkStatus();
```

```
    System.out.println(health + "is good");
```

```
}
```

```
else
```

```
{
```


```
    Fuckin die n6
```

```
}
```


NOT

P	^(not) P
T	F
F	T

* ONLY SINGLE VARIABLE FUNCTION

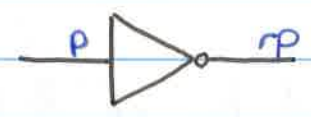

CIRCUIT

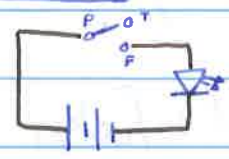


if (!P)
light = on;

OR

pq	prq
FF	F
FT	T
TF	T
TT	T


pq	prq
00	0
01	1
10	1
11	1

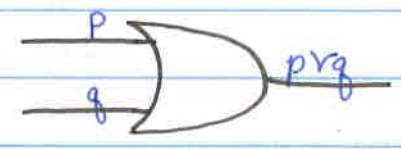

if (p || q)
light = on;

* OR IS INCLUSIVE *


CIRCUIT:

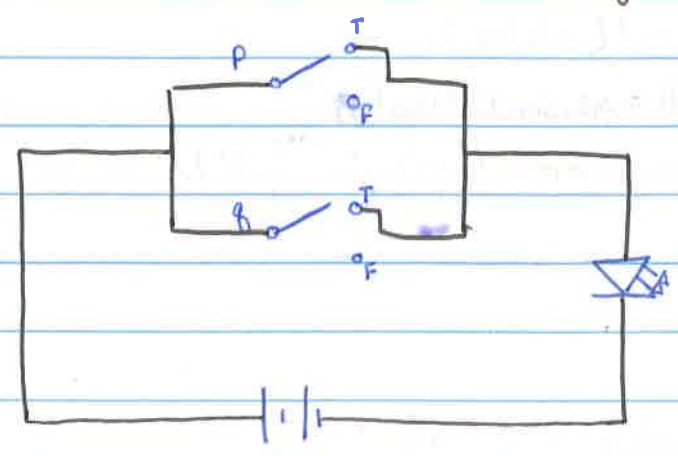

and

p	q	$p \wedge q$
F	F	0
F	T	0
T	F	0
T	T	1


* ONLY IF BOTH ARE TRUE

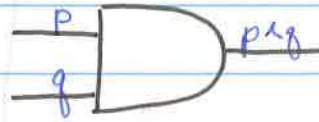

$\text{if}(p \& \& q)$

Light = on;

CIRCUIT:

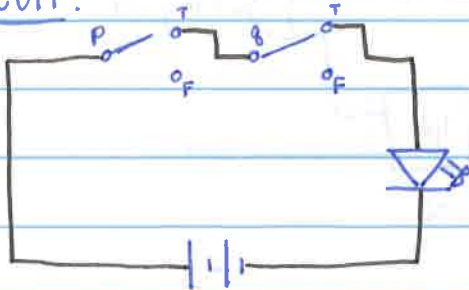

xor

p	q	$p \oplus q$
F	F	0
F	T	1
T	F	1
T	T	0




* USED IN HUNCH FOR
REVERSING POLARITY ON

LA



* EXCLUSIVE (NO TT) *

CIRCUIT:

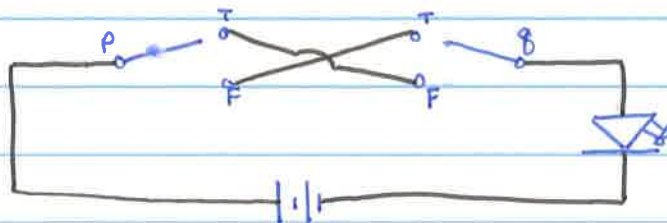

HALF ADDER

X	+	Y	=	C	S
0	+	0	=	0	0
0	+	1	=	0	1
1	+	0	=	0	1
1	+	1	=	1	0

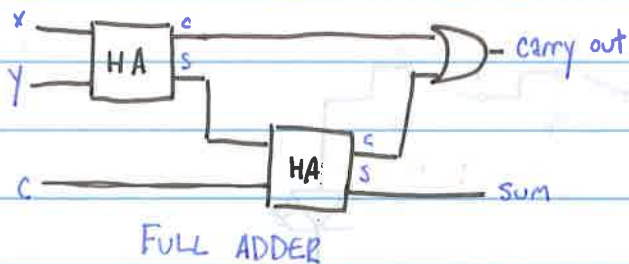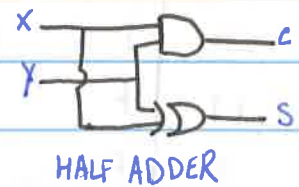

* USE MORE HALF ADDERS TO ADD MORE BITS *