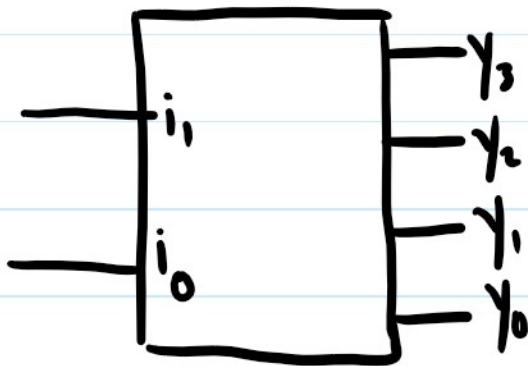


Section 3 - Decoders

Wednesday, June 19, 2019 12:10 PM

• SECTION 3 • • • • DECODERS • • •


• SAME PRINCIPLE AS A MUX



i_1	i_0	out
0	0	y_0
0	1	y_1
1	0	y_2
1	1	y_3

• WE HAVE N INPUTS THAT ACTIVATE A SERIES OF 2^N OUTPUTS.


THE CIRCUIT

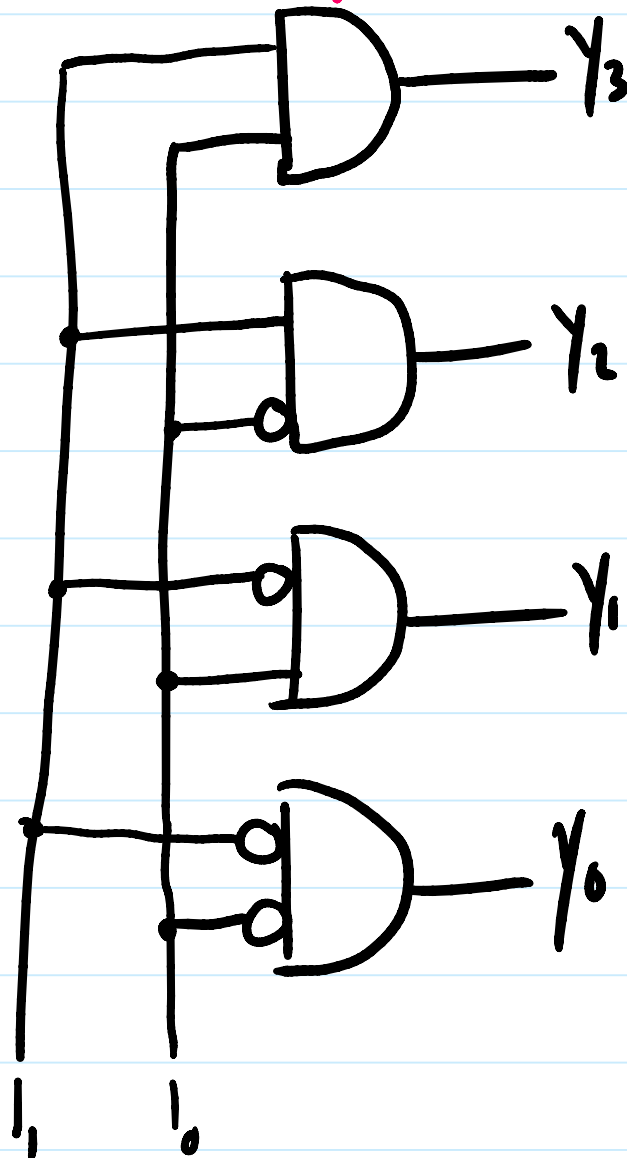

- So IF $1, 0$ is the input then y_3 is the only output set to 1. leaving the others at 0.
- So BASICALLY BINARY \rightarrow BASE 10?


ENABLE INPUT

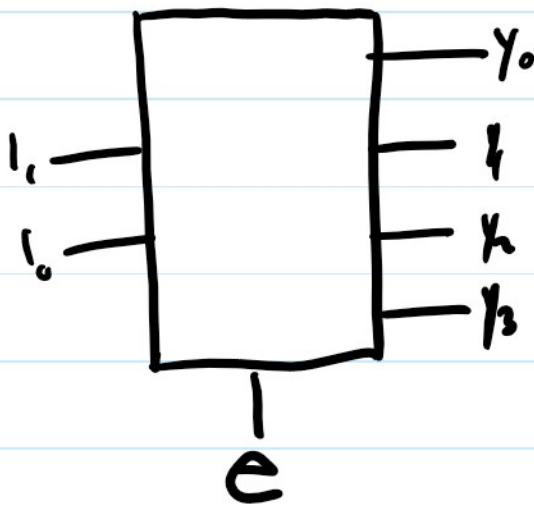- ENABLE INPUT IS SEEN A LOT IN DEVICES.
- THE DEVICE ONLY WORKS IF ENABLE IS 1.



e	i_1	i_0	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	y_0
1	0	1	y_1
1	1	0	y_2
1	1	1	y_3


THE CIRCUIT

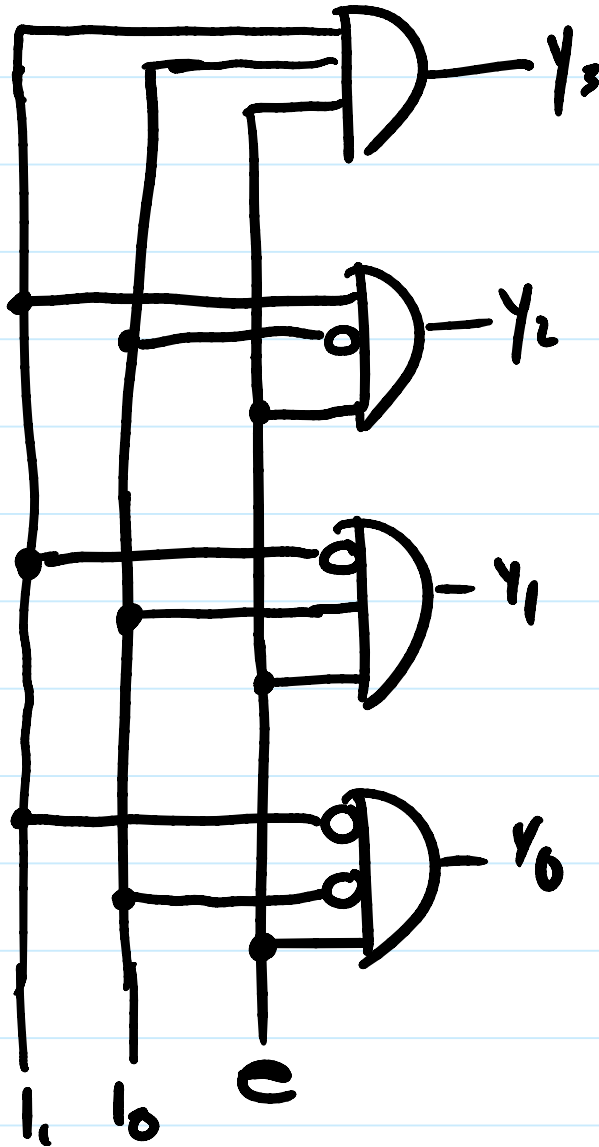

- THE AND GATES CAN ONLY OUTPUT 1 IF E IS 1

DONT CARES

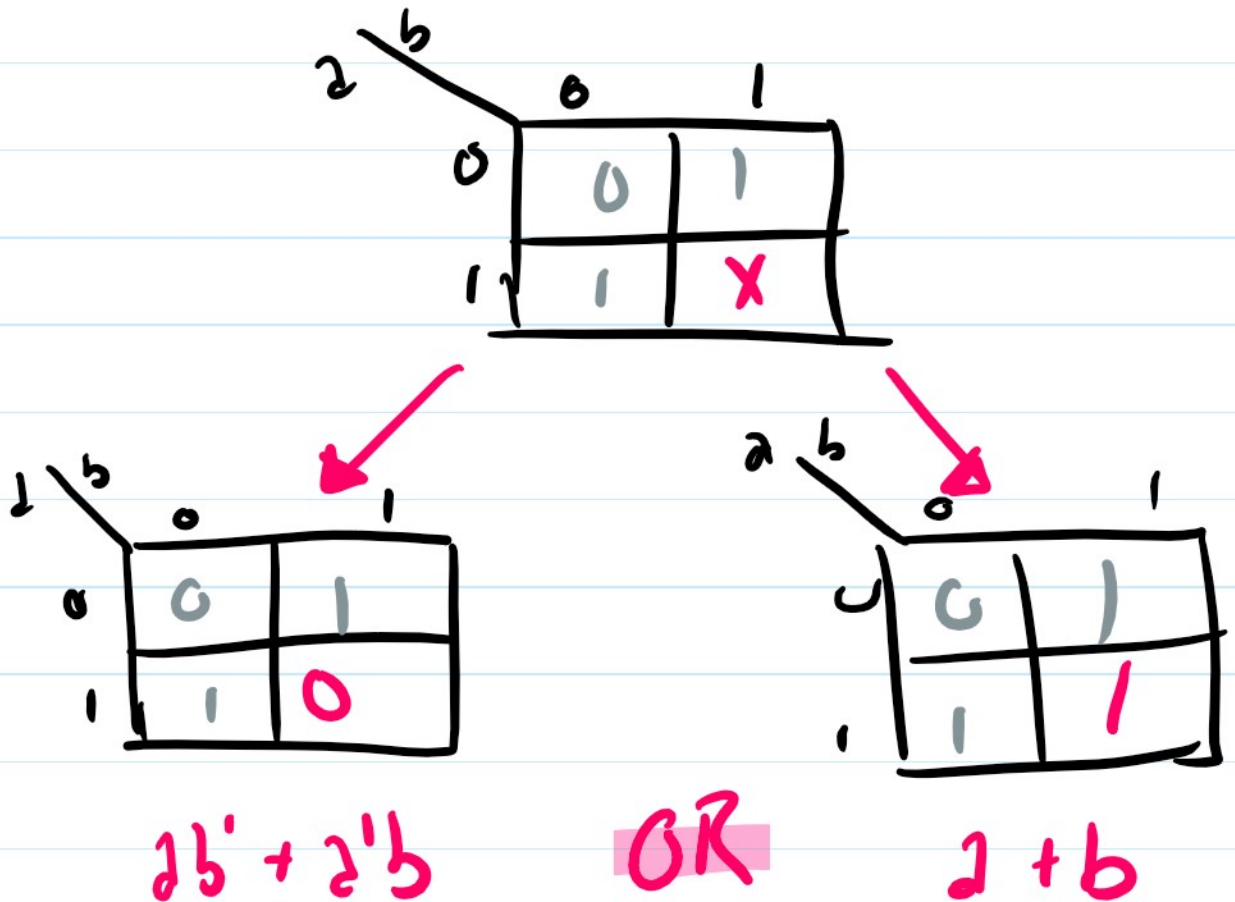- PUT IN MINIMIZING
- PART OF FUNCTION WHERE THE OUTPUT DOESN'T MATTER



- X IS THE "DONT CARE"
- UP TO DESIGNER TO CHOOSE WHAT IF IS BASED ON EASE OF CIRCUIT