


Section 4 - Finite State Machines

Wednesday, June 19, 2019 12:28 PM


• SECTION 4 •

FINITE STATE MACHINES

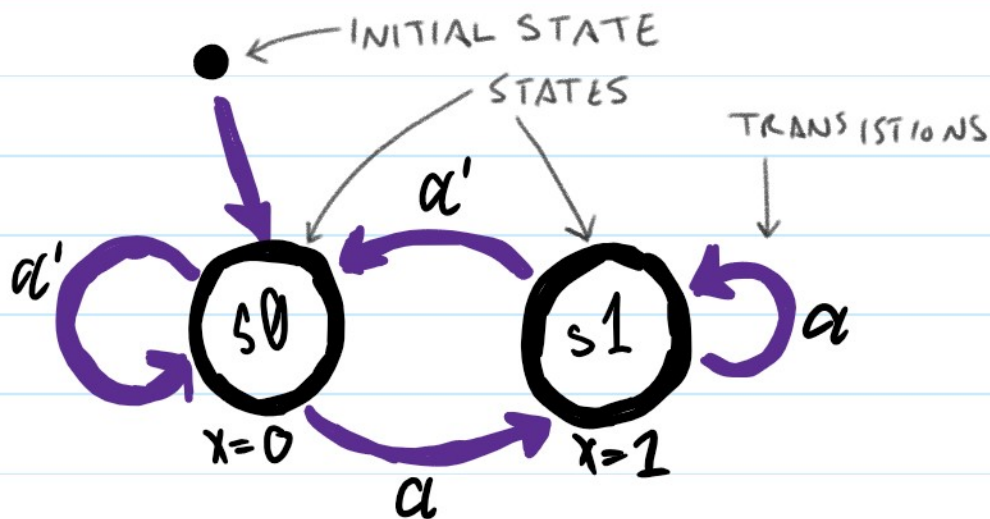- in a combinational circuit, equations are used to describe the behavior
- in a sequential circuit, a **FINITE STATE MACHINE (FSM)** IS USED



INPUTS : α
OUTPUTS : x

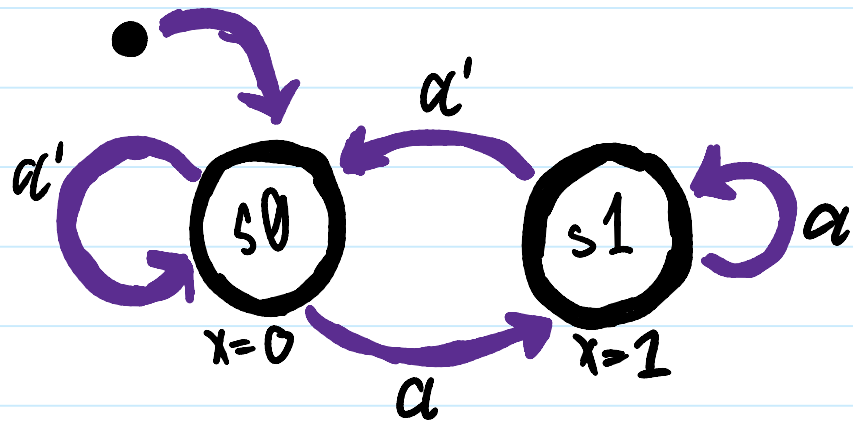

WHAT DOES THIS SAY?

x starts at 0

when α is 1 x becomes 1


when α is 0 x becomes 0

WHENEVER THE CLOCK (CLK) HAS A RISING 1,
THE STATE MACHINE WILL ADVANCE

- DESCRIBING A SYSTEMS BEHAVIOR. IS
KNOWN AS **CAPTURING** BEHAVIOR
WITH A FSM


FSMs TO CIRCUITS

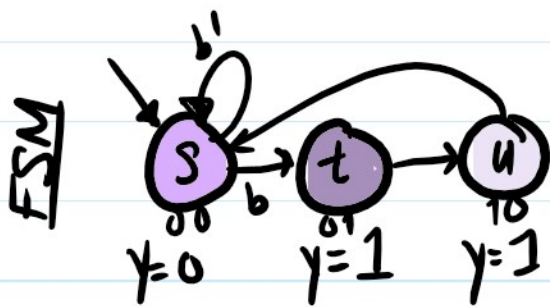- AN EQUATION CAN BE CONVERTED TO A COMBINATIONAL CIRCUIT
- AN FSM CAN BE CONVERTED TO A SEQUENTIAL CIRCUIT CALLED A **CONTROLLER**
- A CONTROLLER CONSISTS OF A REGISTER AND A LOGIC BLOCK
- THE REGISTER STORES THE STATE
 - ↳ THIS MAKES IT A **STATE REGISTER**
- THE LOGIC COMPUTES
 - ↳ OUTPUT BASED ON PRESENT STATE
 - ↳ NEXT STATE BASED ON INPUTS AND PRESENT STATE



	p1	p0	b	n1	n0	y
s	0	0	0	0	0	0
	0	0	1	0	1	0
t	0	1	0	1	0	1
	0	1	1	1	0	1
u	1	0	0	0	0	1
	1	0	1	0	0	1
next	1	1	0	0	0	0
	1	1	1	0	0	0

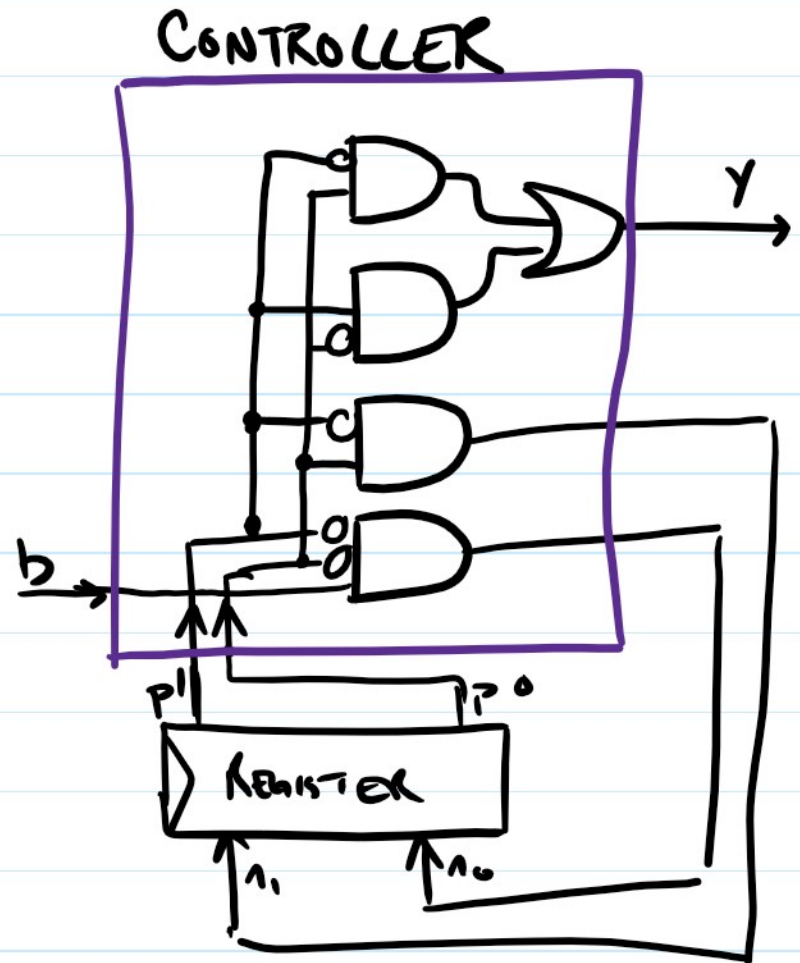Present state: p1, p0
 Input: b
 Next state: n1, n0
 Output: y



- THE CONTROLLER'S HIGH LEVEL VIEW IS CALLED THE ARCHITECTURE
- EACH STATE IS GIVEN A BIT ENCODING TO BE USED