•SECTION 2•
MULTIPLIERS

• • • • •   • • • •

MULTIPLIER - Multiplies 2 N-BIT numbers into a 2N-bit output

4-bit multiplier